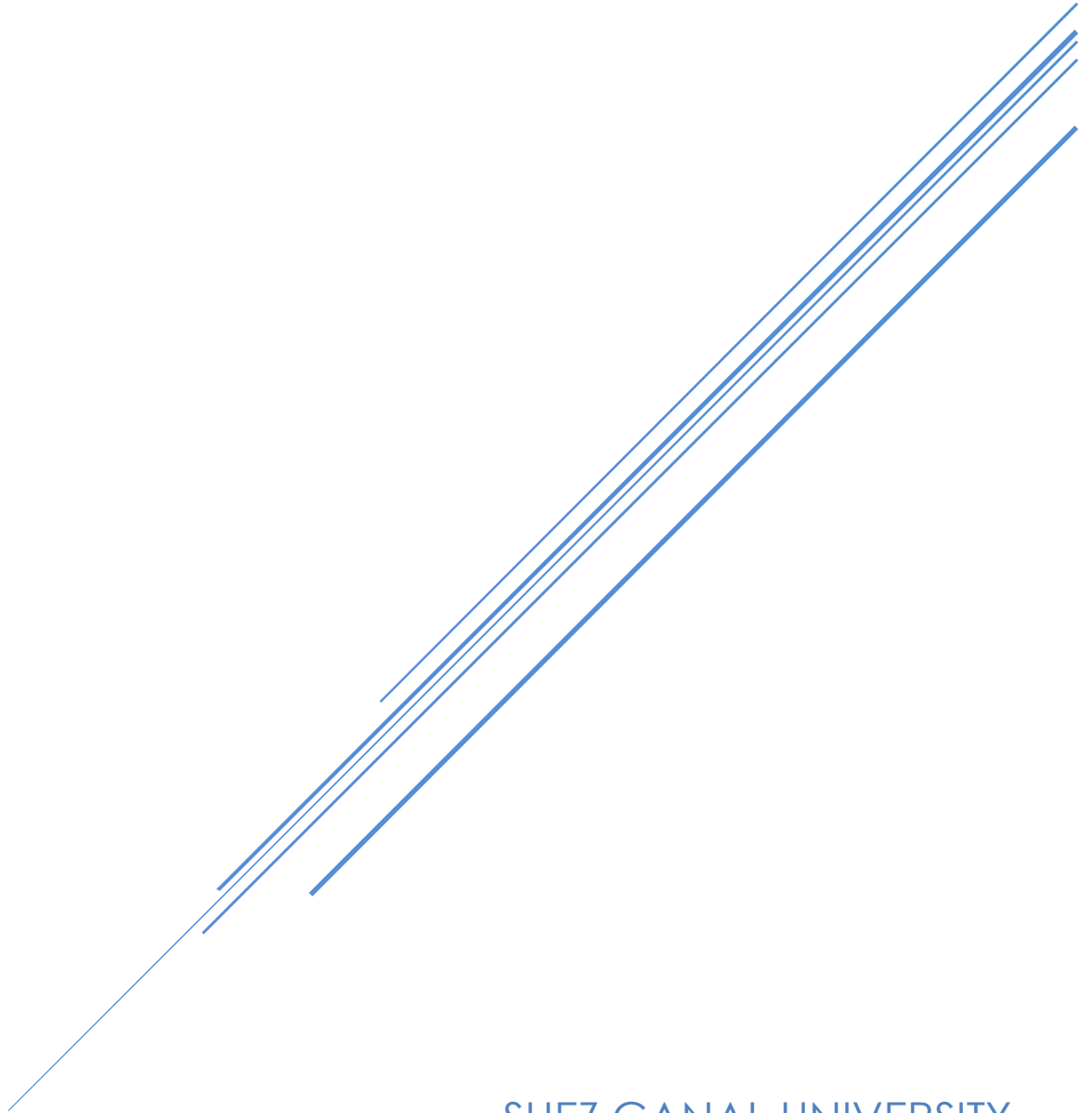


SINGLE ENDED COMMON SOURCE AMPLIFIER



SUEZ CANAL UNIVERSITY

Yossef Nada

Design a single ended amplifier (choose common source with resistive load) to achieve the following specs

Spec.	
DC Gain	20 dB
BW	$\geq 1 \text{ GHz}$
Power Consumption	$\leq 0.5 \text{ mW}$
Cap Load	50 fF

Design ②

Specs gain 20 dB
 BW $\geq 1 \text{ GHz}$
 Power $\leq 0.5 \text{ mW}$
 Cap. Load 50 fF

Then,

$$I \leq \frac{0.5 \text{ mW}}{1.2} \leq 400 \text{ nA}$$

we chose $V_{DD} = 1.2 \text{ V}$

$$GBW = \frac{g_m}{2\pi C_L} = 10 \times 10^9$$

$$\therefore g_m = 3.14 \text{ mS}$$

$$\frac{g_m}{I_D} = 7.85 \quad \text{up to } 8$$

$$V^* = 0.25 \text{ V}$$

let $V_{DS} = \frac{V_{DD}}{2} = 0.6 \text{ V}$ $\therefore R_D = \frac{0.6}{400 \mu} = 1500 \Omega$

" we will sweep V_{GS} over $L = 100 \text{ nm}, 150 \text{ nm}, 200 \text{ nm}, 175 \text{ nm}, 300 \text{ nm}$

" $A_v = g_m R_{out} \approx 10$

take $g_m = 3.2 \text{ mS}$

But This g_m would need $R_{out} \approx 3000 \Omega$ to get The specified gain

" $R_D = 1500 \Omega$


put $\frac{g_m}{I_D} = 20$ " $g_m = 8 \text{ mS}$

" $R_{out} \approx 1250$

" $\frac{1}{R_D} + g_{ds} \leq \frac{1}{1250}$ " $g_{ds} \leq \frac{1}{1500}$

" $\frac{g_m}{g_{ds}} \approx 60$

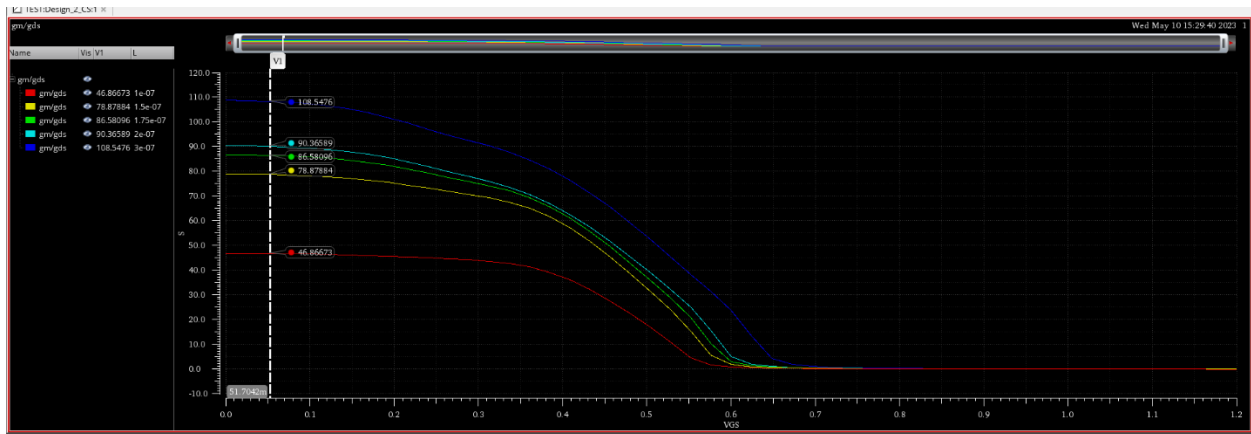Studying $\frac{g_m}{g_{ds}}$ curves we found that $L = 150 \text{ nm}$



$$\frac{g_m}{I_D} = 20 \quad \therefore V^* = 0.1 \text{ V}$$

$$\therefore V_{GSQ} = 344.233 \text{ mV}$$


$$I_{DQ} = 55.0387 \text{ uA}$$

$$g_{mQ} = 1.0914 \text{ mS}$$

$$\therefore \text{at } W = 10 \text{ u} \quad I_{DQ} = 55.0387 \text{ uA}$$

$$W = ? \quad I = 400 \text{ uA}$$

$$\therefore W = 72.676 \text{ um}$$

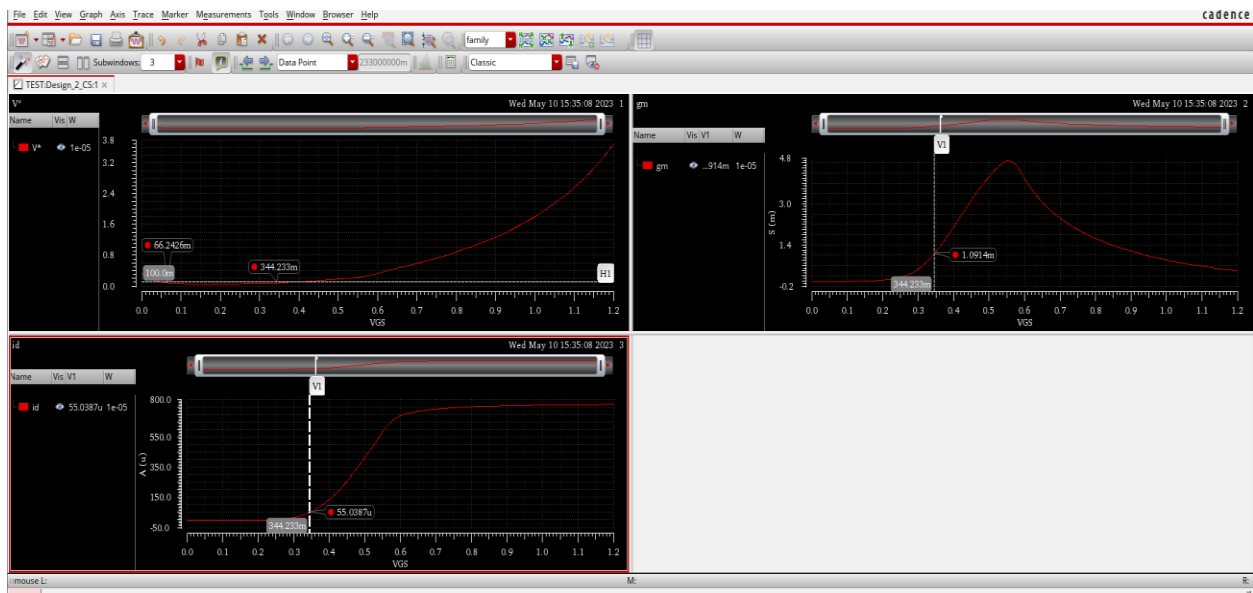

discussing gain and BW

$$BW = 1.322 \text{ G}$$

$$\text{Gain} = 18.66 \text{ dB}$$

Managing R_D : put $R_D = 1800 \Omega$



$$\text{gain} = 19.67 \text{ dB}$$

$$BW = 1.133 \text{ G}$$

put $R_D = 1950 \Omega$

$$BW = 1.082 \text{ G}$$

$$\text{gain} = 20.07 \text{ dB}$$

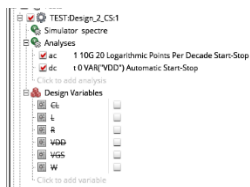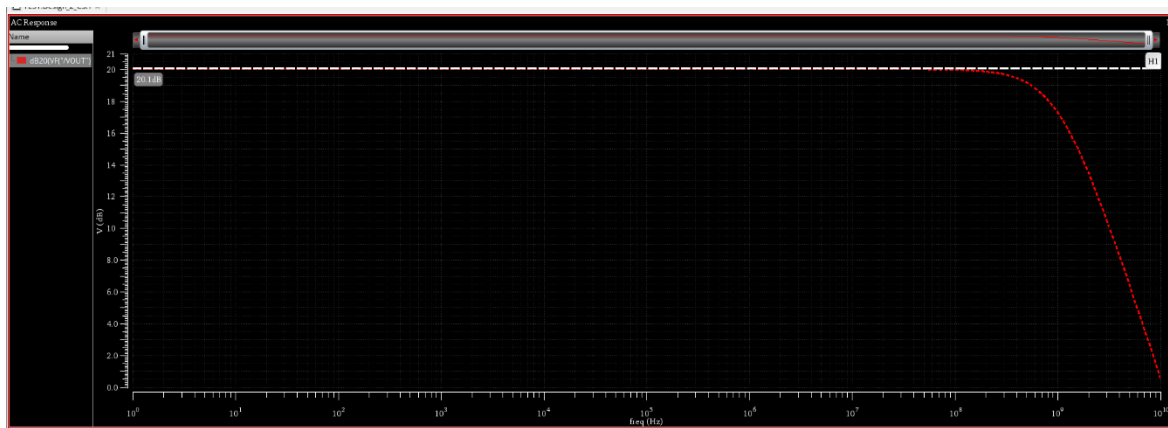

Test	Output	Nominal	Spec	Weight	Past/Fail
TEST-Design_2_CS1	VTH				
TEST-Design_2_CS1	V*				
TEST-Design_2_CS1	gmVgds				
TEST-Design_2_CS1	id				
TEST-Design_2_CS1	vth	394.5m			
TEST-Design_2_CS1	gm				
TEST-Design_2_CS1	VOUT				
TEST-Design_2_CS1	BW	1.062G			

Species desired

obtained

Gain = 20 dB

Gain = 20.07 dB

BW $\approx 1 \text{ GHz}$

$$B_w = 1.062 \text{ GHz}$$

Power $\leq 0.5\text{mw}$

power = 0.3822 mW

desired speed achieved

