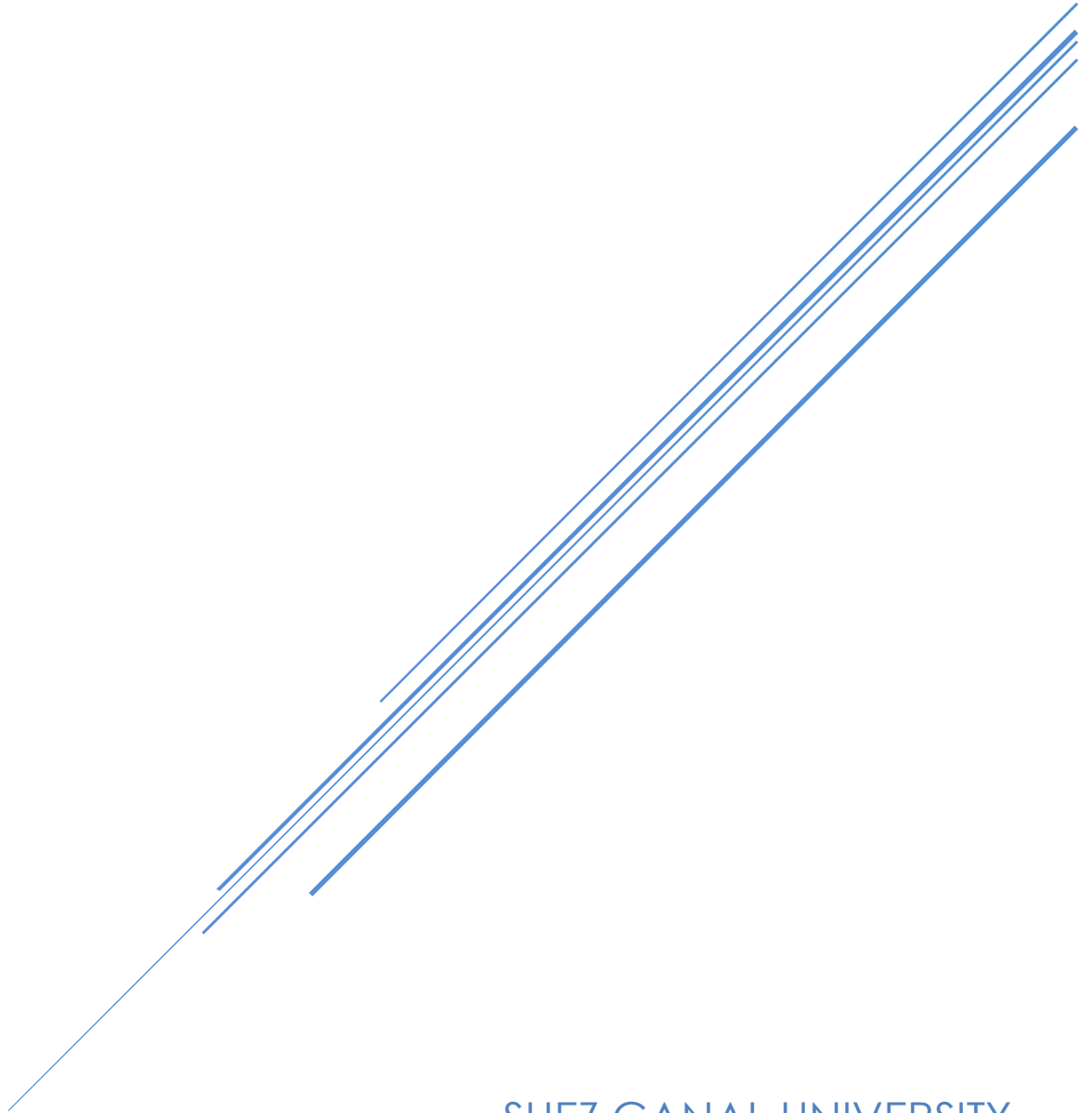


# INTEGRATED CIRCUITS 1

## LAB03



SUEZ CANAL UNIVERSITY

Yossef Ibrahim Abdel Aziz El Sayed Nada

## Part 1: Sizing Chart

- 1) We can show that the intrinsic gain of a MOSFET is given by

$$|A_v| \approx g_m r_o = \frac{2I_D}{V_{ov}} \times \frac{V_A}{I_D} = \frac{2V_A}{V_{ov}}$$

Interestingly, the gain only depends on  $\lambda$  and  $V_{ov}$ . However, to derive this expression we used  $g_m = \frac{2I_D}{V_{ov}}$  which is based on the square-law. For a real MOSFET, if we compute  $V_{ov}$  and  $\frac{2I_D}{g_m}$  they will not be equal. Let's define a new parameter called V-star ( $V^*$ ) which is calculated from actual simulation data using the formula

$$V^* = \frac{2I_D}{g_m} \leftrightarrow g_m = \frac{2I_D}{V^*}$$

For a square-law device,  $V^* = V_{ov}$ , however, for a real MOSFET they are not equal. The actual gain is now given by


$$|A_v| \approx \frac{2V_A}{V^*}$$

The lower the  $V^*$  the higher the gain, but the larger the area and the lower the speed. An often used sweet-spot that provides good compromise between different trade-offs is  $V^* = 200\text{mV}$ .

- 2) We want to design CS and cascode amplifiers with the parameters below.

Parameter	0.13um CMOS	0.18um CMOS
$L^1$	$0.5\mu\text{m}$	$0.5\mu\text{m}$
$V^*$	$200\text{mV}$	$200\text{mV}$
Supply	$1.2\text{V}$	$1.8\text{V}$
Current consumption	$20\mu\text{A}$	$20\mu\text{A}$

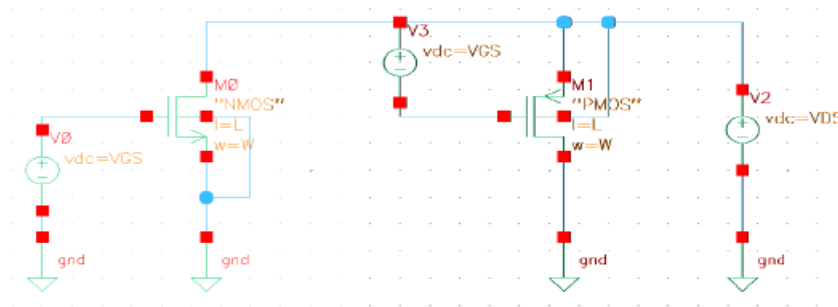
- 3) The remaining variable in the design is to calculate  $W$ . Since the square-law is not accurate, we cannot use it to determine the sizing. Instead, we will use a sizing chart generated from simulation. Create a testbench for NMOS transistor as shown below (we will use NMOS only in this lab). Use  $W = 10\mu\text{m}$  (we will understand why shortly) and  $L = 0.5\mu\text{m}$  (the same  $L$  selected before).



- 4) Sweep VGS from 0 to  $\approx V_{TH} + 0.4\text{V}$  with 10mV step. Set  $V_{DS} = V_{DD}/2$ .
- 5) We want to compare  $V^* = 2I_D/g_m$  and  $V_{ov} = V_{GS} - V_{TH}$  by plotting them overlaid. Use the calculator to create expressions for  $V^*$  and  $V_{ov}$ . You can save the expressions to reuse them later.
- 6) Plot  $V^*$  and  $V_{ov}$  overlaid vs VGS. Make sure the y-axis of both curves has the same range. You will notice that at the beginning of the strong inversion region,  $V^*$  and  $V_{ov}$  are relatively close to each other (i.e., square-law is relatively valid). For deep strong inversion (large  $V_{ov}$ : velocity saturation and mobility degradation) or weak inversion (near-threshold and subthreshold operation) the behavior is quite far from the square-law.
- 7) An often used sweet-spot that provides good compromise between different trade-offs is  $V^* = 200\text{mV}$ . On the  $V^*$  and  $V_{ov}$  chart locate the point at which  $V^* = 200\text{mV}$ . Find the corresponding  $V_{ovQ}$  and  $V_{GSQ}$ .
- 8) Plot  $I_D$ ,  $g_m$ , and  $g_{ds}$  vs  $V_{GS}$ . Find their values at  $V_{GSQ}$ . Let's name these values  $I_{DX}$ ,  $g_{mX}$ , and  $g_{dsX}$ .
- 9) Now back to the assumption that we made that  $W = 10\mu\text{m}$ . This is not the actual value that we will use for our design. But the good news is that  $I_D$  is always proportional to  $W$  irrespective of the operating region and the model of the MOSFET (regardless square-law is valid or no). Thus, we can use ratio and proportion (cross-multiplication) to determine the correct width at which the current will be  $I_{DQ} = 20\mu\text{A}$  as given in the specs. Calculate  $W$  as shown below.

$W$	$I_D$
$10\mu\text{m}$	$I_{DX} @ V_{GSQ}^*$ (from the chart)
?	$I_{DQ} = 20\mu\text{A}$ (from the specs)

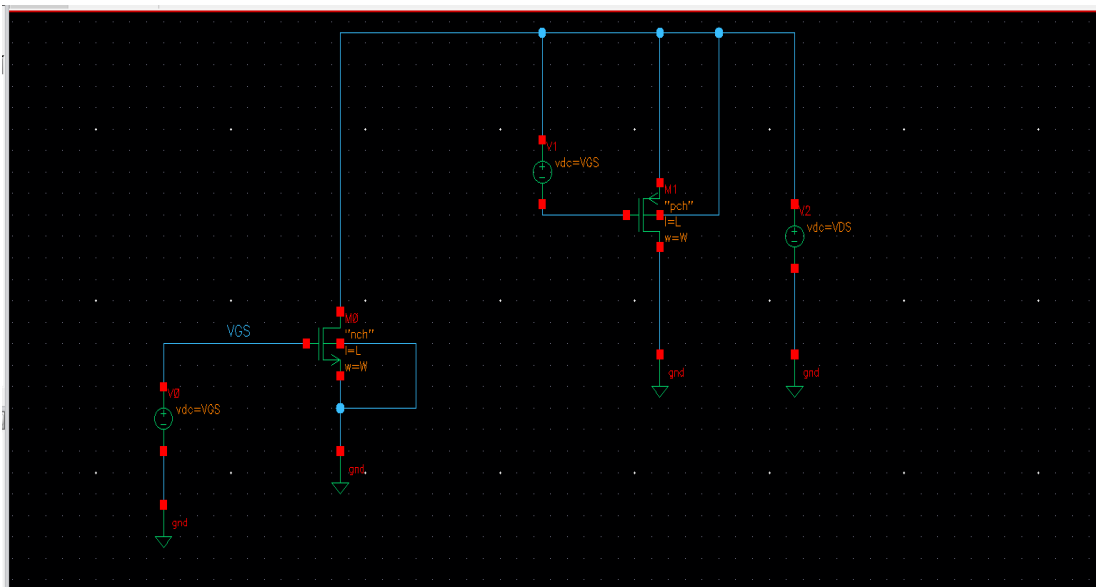- 10) Now we are almost done with the design of the amplifier. Note that  $g_m$  is also proportional to  $W$  as long as  $V_{ov}$  is constant. On the other hand,  $r_o = 1/g_{ds}$  is **inversely** proportional to  $W$  ( $I_D$ ) as long as  $L$  is constant. Before leaving this part, calculate  $g_{mQ}$  and  $g_{dsQ}$  using ratio and proportion (cross-multiplication).



$$L = 0.5 \mu\text{m}$$

$$V^* = 200 \text{ mV}$$

$$\text{Supply} = 1.8 \text{ V}$$

$$\text{Current} = 20 \mu\text{A}$$

Consump.

$$V_{th} = 441 \text{ mV}$$

$$\text{at } V^* = 200 \text{ mV} \quad \left. \begin{array}{l} \rightarrow V_{ovQ} = 202.983 \text{ mV} \\ \rightarrow V_{GSQ} = 643.977 \text{ mV} \end{array} \right\}$$

$$I_{D_x} = 96.0691 \mu\text{A}$$

$$g_{m_x} = 959.32 \mu\text{S}$$

$$g_{ds_x} = 9.7245 \mu\text{S}$$

$$W \propto I_D$$

$$10 \mu\text{m} \quad 96.0691 \mu\text{A}$$

$$? \quad 20 \mu\text{A}$$

$$\therefore \boxed{W = 2.08183 \mu\text{m}}$$




→ This is different from the Square Law


$$g_m \propto W$$

at Const.

$$\frac{g_{m1}}{g_{m2}} = \frac{W1}{W2} \quad \frac{959.32}{g_{m2}} = \frac{10}{2.0818} \quad \therefore g_{m2} = 201.16 \mu\text{S}$$

Outputs Setup   Run Preview   Results   Diagnostics						
Detail						
Test	Output	Nominal	Spec	Weight	Pass/Fail	
model_file_added_MOS_lib:Lab03_Part01:1	VTH	441m				
model_file_added_MOS_lib:Lab03_Part01:1	V*					
model_file_added_MOS_lib:Lab03_Part01:1	Vov					
model_file_added_MOS_lib:Lab03_Part01:1	gm					
model_file_added_MOS_lib:Lab03_Part01:1	gds					
model_file_added_MOS_lib:Lab03_Part01:1	id					

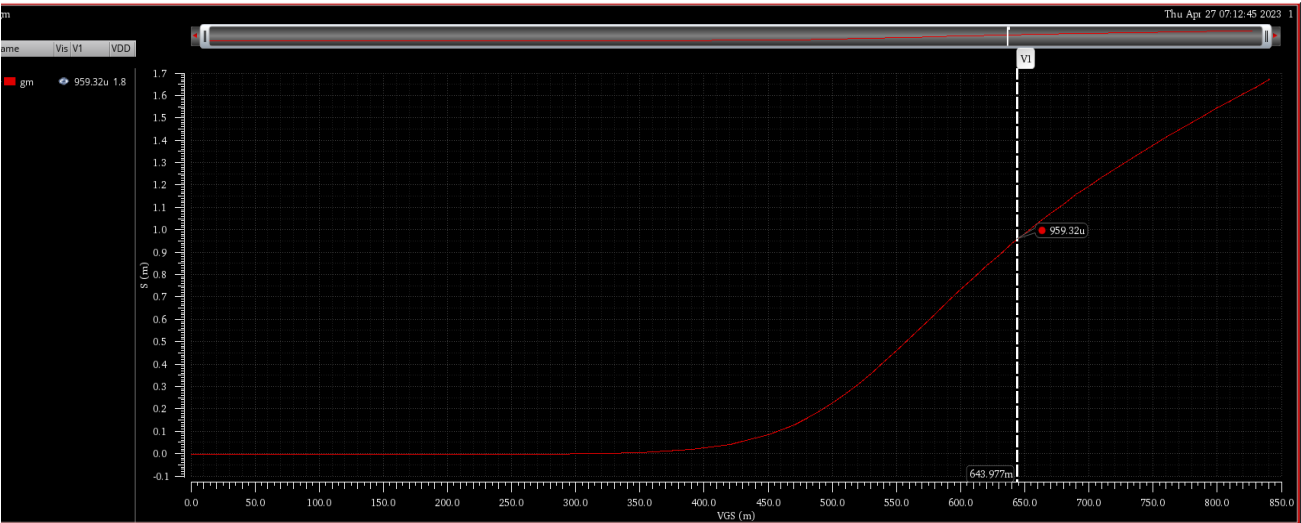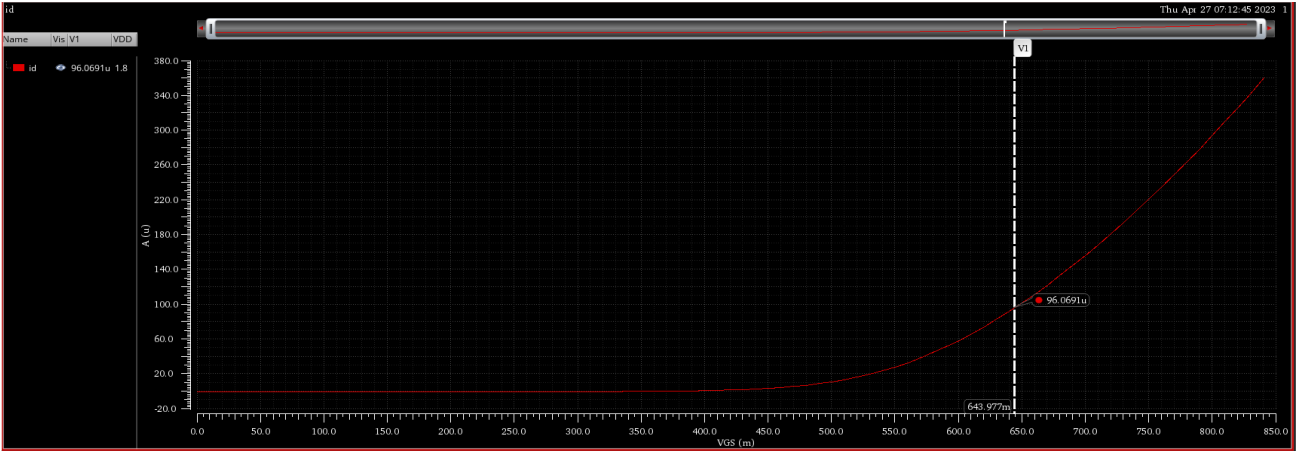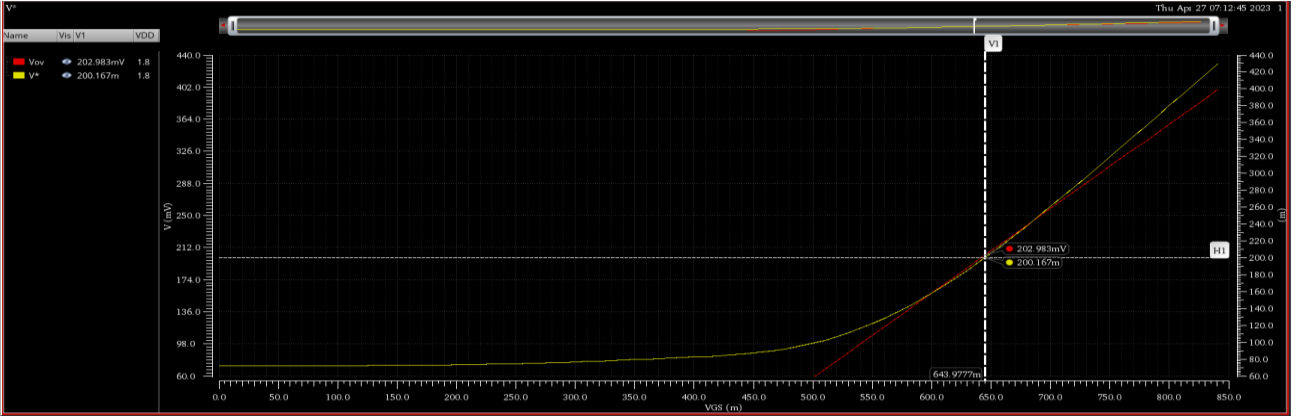

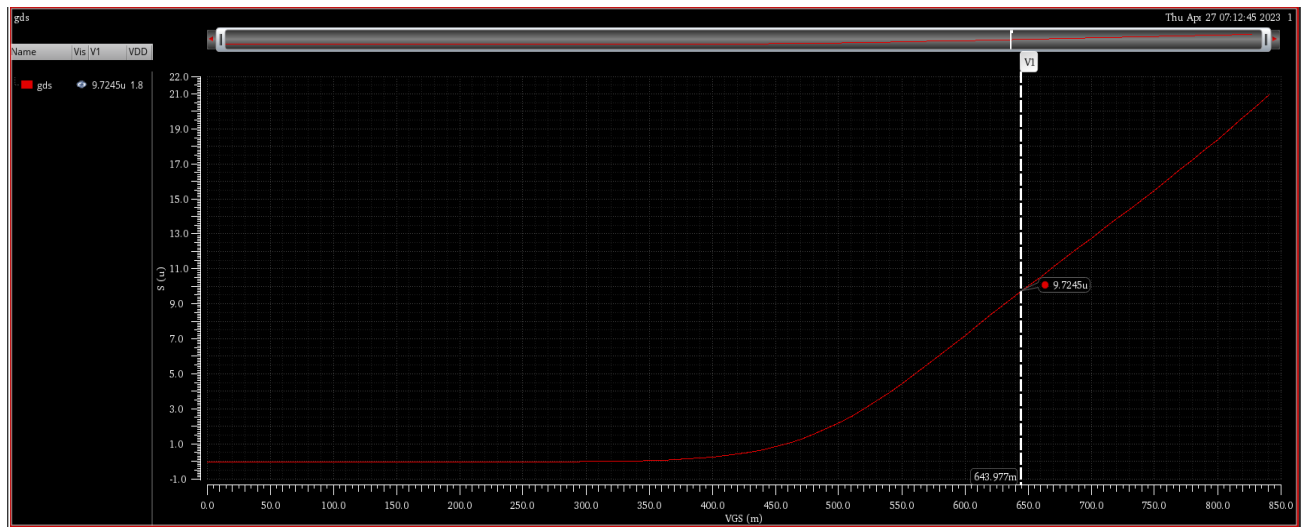

$$g_{ds} = \frac{I_D}{V_A} = I_D \lambda$$

So at  $L$  Const.

$$g_{ds} \propto I_D$$

$$g_{ds} \propto W$$

$$\therefore \frac{g_{ds1}}{g_{ds2}} = \frac{W_1}{W_2}$$

$$\frac{9.7245}{g_{ds2}} = \frac{10}{2.0818} \therefore g_{ds2} = 2.0244 \text{ } \mu\text{S}$$

parameters

$I_{DQ}$	20 $\mu\text{A}$
$g_{mQ}$	199.7 $\mu\text{S}$
$g_{dsQ}$	2.0244 $\mu\text{S}$
$r_o$	493.97 $\text{k}\Omega$
$W$	2.0818 $\mu\text{m}$
$L$	0.5 $\mu\text{m}$
Supply Volt	1.8 $\text{V}$
$V^*$	200 $\text{mV}$
$V_{ovQ}$	202.983 $\text{mV}$
$V_{GSQ}$	643.977 $\text{mV}$



## PART 2: Cascode for Gain


### 1. OP Analysis

- 1) Create a new cell and schematic. Construct the circuit shown below. Use  $I_B = 20\mu A$ ,  $L = 0.5\mu m$ ,  $W$  as selected in Part 1, and  $C_L = 1pF$ .
- 2) Choose  $V_B$  (the cascode device bias voltage) such that M2 has  $V_{DS} \approx V^* + 100mV$  (you may sweep  $V_B$  and plot  $V_{DS}$  vs  $V_B$  to help you choose a good value for  $V_B$ ).
- 3) We need to bias transistors in saturation; however, the output node is a high impedance node; thus, it is difficult to control its DC voltage. As a workaround in simulation, we use a feedback loop and resistors with different resistances in DC/AC to change the circuit connections in DC/AC simulations (use the AC property in ideal\_resistor). The input transistor is diode connected for DC simulation (always in saturation), while in AC simulation the feedback is disconnected, and the AC input source is connected. Set the feedback resistance  $1m\Omega$  DC and  $1T\Omega$  AC and set the source resistance oppositely. We will study how to do biasing practically later in this course inshaAllah.
- 4) Simulate the DC OP point of the above CS and cascode amplifiers. Report a snapshot showing the following parameters for M1, M2 and M3 in addition to DC node voltages clearly annotated.


ID
VGS
VDS
VTH
VDSAT
GM
GDS
GMB
CDB
CGD
CGS
CSB
Region

"vdsat" is the minimum drain-source voltage required to bias the transistor in saturation. It is equal to  $V_{ov}$  for a square-law device. It is also referred to as "vdss" (drain-source saturation voltage).

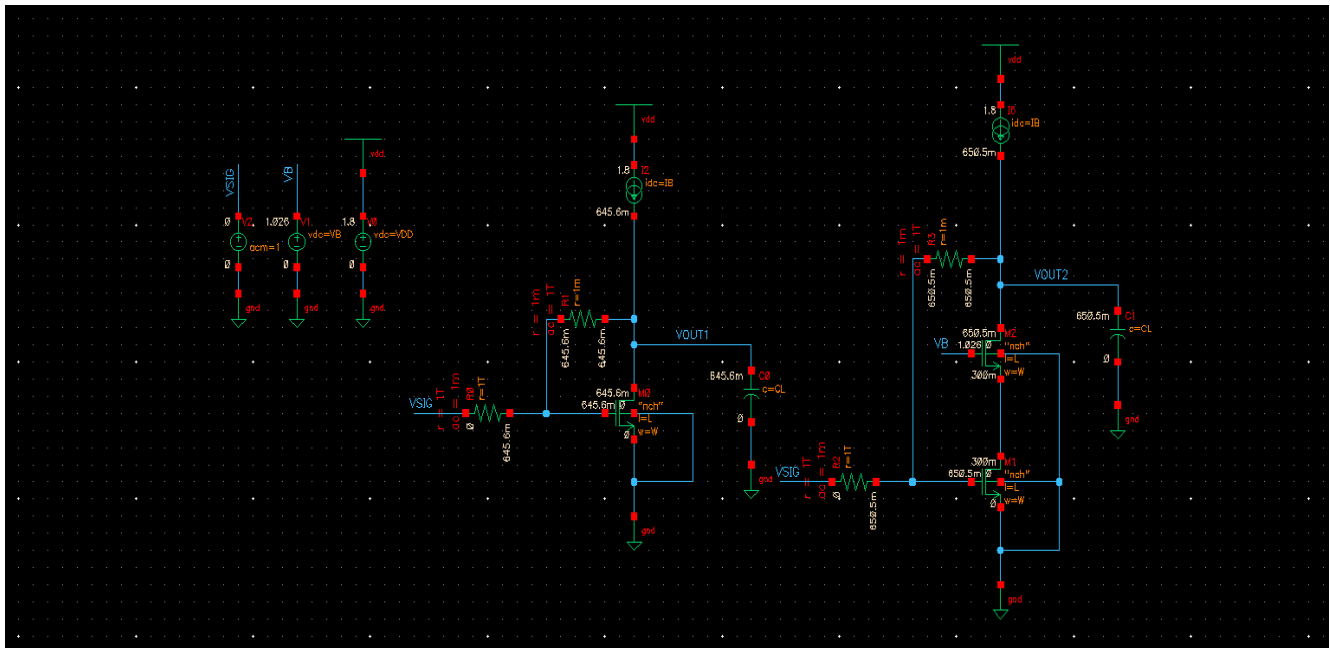- ✓ 6) Check that all transistors operate in saturation.
- ✓ 7) Do all transistors have the same vth? Why?
- ✓ 7) What is the relation ( $\ll, <, =, >, \gg$ ) between gm and gds?
- ✓ 8) What is the relation ( $\ll, <, =, >, \gg$ ) between gm and gmb?
- ✓ 9) What is the relation ( $\ll, <, =, >, \gg$ ) between cgs and cgd?
- ✓ 10) What is the relation ( $\ll, <, =, >, \gg$ ) between csb and cdb?



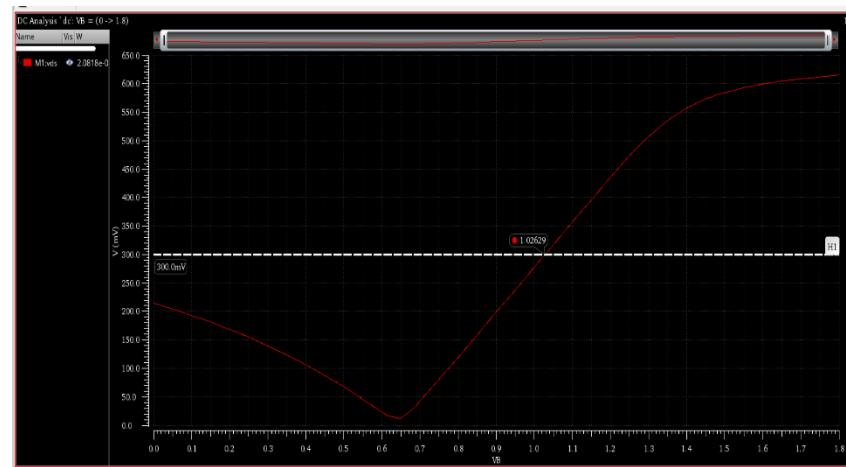$V_{DS} \approx V^* + 100 \text{ mV} \approx 300 \text{ mV}$   
 $\downarrow$   
 M1  
 From The graph  $V_B \approx 1.02629 \text{ V}$



5) all transistors operate in sat. as they all have the region 2

Test	Output	Nominal	Spec	Weight	Pass/Fail
model_file_added_MOS_ItbLab03_Part02.1	getData("M2region") result "dcOp")	2			
model_file_added_MOS_ItbLab03_Part02.1	getData("M1region") result "dcOp")	2			
model_file_added_MOS_ItbLab03_Part02.1	getData("M0region") result "dcOp")	2			

Snap shots required in Question 4:

	1
W	2.082E-6
M0: id	20.00E-6
M0: vgs (V)	645.6E-3
M0: vds (V)	645.6E-3
M0: vth (V)	442.1E-3
M0: vdsat (V)	155.1E-3
M0: vdss (V)	155.1E-3
M0: gm	199.7E-6
M0: gds	2.253E-6
M0: gmb	53.96E-6
M0: cdb	-1.748E-15
M0: cgd	-983.0E-18
M0: cgs	-7.497E-15
M0: csb	-3.743E-15
M0: region	2

	1
W	2.082E-6
M1: id	20.00E-6
M1: vgs (V)	650.5E-3
M1: vds (V)	300.0E-3
M1: vth (V)	444.7E-3
M1: vdsat (V)	156.7E-3
M1: vdss (V)	156.7E-3
M1: gm	196.3E-6
M1: gds	4.440E-6
M1: gmb	53.09E-6
M1: cdb	-1.910E-15
M1: cgd	-1.011E-15
M1: cgs	-7.508E-15
M1: csb	-3.735E-15
M1: region	2

	1
W	2.082E-6
M2: id	20.00E-6
M2: vgs (V)	726.3E-3
M2: vds (V)	350.5E-3
M2: vth (V)	530.5E-3
M2: vdsat (V)	160.2E-3
M2: vdss (V)	160.2E-3
M2: gm	199.8E-6
M2: gds	3.608E-6
M2: gmb	48.50E-6
M2: cdb	-1.759E-15
M2: cgd	-997.6E-18
M2: cgs	-7.444E-15
M2: csb	-3.327E-15
M2: region	2

$$6) \quad V_{th} = \underline{V_{gs}} - \underline{V_{dsat}}$$

these values differ from one transistor to the other

as we can see the first two transistors are close to each other in  $V_{th}$  as their body effect can be neglected by the third one has body effect as the body is not connected to the source M2

$$7) \quad g_m \gg g_{ds} \quad \text{from 50 to 100 times}$$

$$8) \quad g_m > g_{mb} \quad 3-4 \text{ times}$$

$$9) \quad g_{gs} > g_d \quad 3-5 \text{ times}$$

$$10) \quad g_{sb} > g_{db} \quad 3-5 \text{ times}$$





## 2. AC Analysis


- ✓1) Create a new simulation configuration. Perform AC analysis (1Hz:10GHz, logarithmic, 10points/decade) to simulate gain and bandwidth.
- ✓2) Use calculator to create expressions for circuit parameters (DC gain, BW, GBW, and UGF) and export them to adexl.
  - ➔ Cadence Hint: Use the following expressions in the calculator, and send them to adexl to quickly calculate circuit parameters.

Type	Expression/Signal/File	EvalType	Plot
expr	dB20(VF("/vout1"))	point	✓
expr	ymin(dB20(VF("/vout1")))	point	✓
expr	ymin(mag(VF("/vout1")))	point	✓
expr	bandwidth(VF("/vout1") 3 "low")	point	✓
expr	gainBwProd(VF("/vout1"))	point	✓
expr	dB20(VF("/vout2"))	point	✓
expr	ymin(dB20(VF("/vout2")))	point	✓
expr	ymin(mag(VF("/vout2")))	point	✓
expr	bandwidth(VF("/vout2") 3 "low")	point	✓
expr	gainBwProd(VF("/vout2"))	point	✓

- ✓3) Report the Bode plot (magnitude) of CS and cascode **appended on the same plot**.
- ✓4) Using small signal parameters from OP simulation, perform hand analysis to calculate DC gain, BW, and GBW of both circuits.
- ✓5) Report a table comparing the DC gain, BW, UGF, and GBW of both circuits from simulation and hand analysis.
- ✓6) Comment on the results.

Test	Output	Nominal	Spec	Weight	Pass/Fail
model_file_added_MOS_1b03_Par02-1	dB20(VF("/vout1"))				
model_file_added_MOS_1b03_Par02-1	ym(dB20(VF("/vout1")))	38.95			
model_file_added_MOS_1b03_Par02-1	mag(VF("/vout1"))				
model_file_added_MOS_1b03_Par02-1	ym(mag(VF("/vout1")))	88.63			
model_file_added_MOS_1b03_Par02-1	bandwidth(VF("/vout1") 3 "L")	358k			
model_file_added_MOS_1b03_Par02-1	gainBwProd(VF("/vout1"))	31.8M			
model_file_added_MOS_1b03_Par02-1	dB20(VF("/vout2"))				
model_file_added_MOS_1b03_Par02-1	ym(dB20(VF("/vout2")))	69.79			
model_file_added_MOS_1b03_Par02-1	mag(VF("/vout2"))				
model_file_added_MOS_1b03_Par02-1	ym(mag(VF("/vout2")))	3.086k			
model_file_added_MOS_1b03_Par02-1	bandwidth(VF("/vout2") 3 "L")	9.901k			
model_file_added_MOS_1b03_Par02-1	gainBwProd(VF("/vout2"))	30.62M			

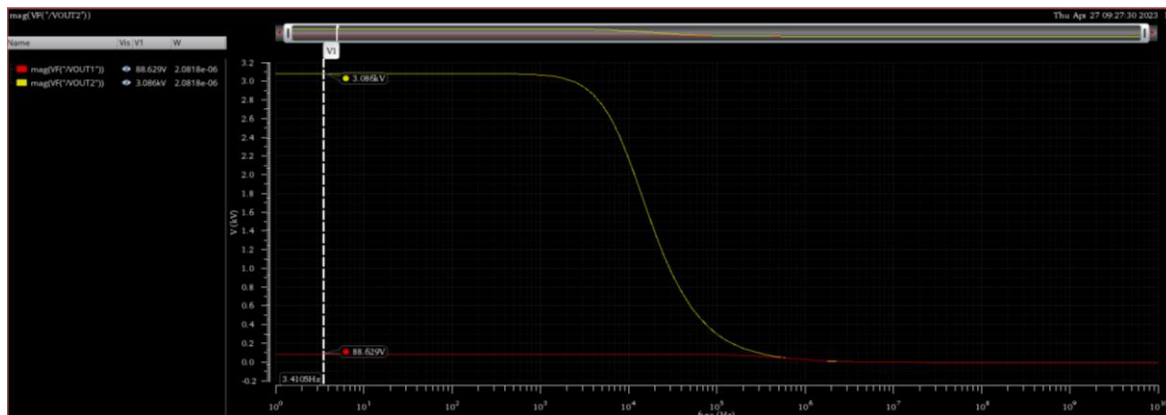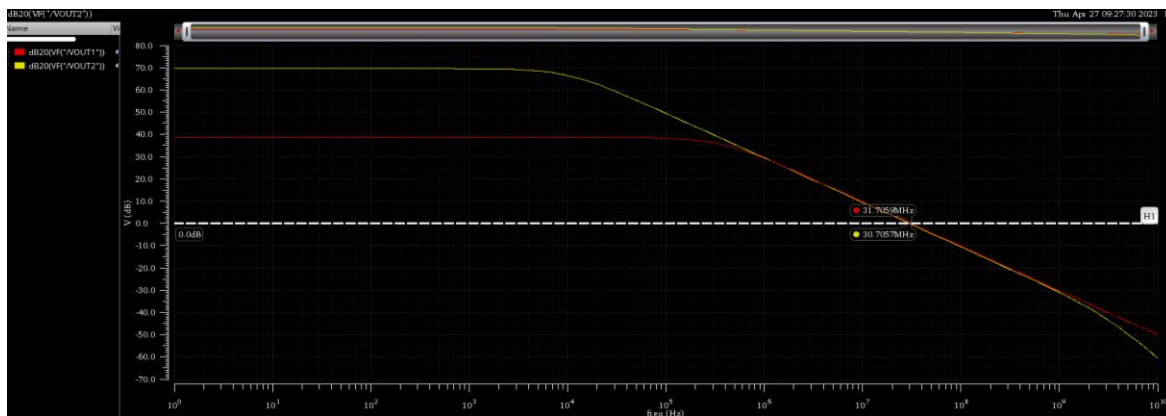


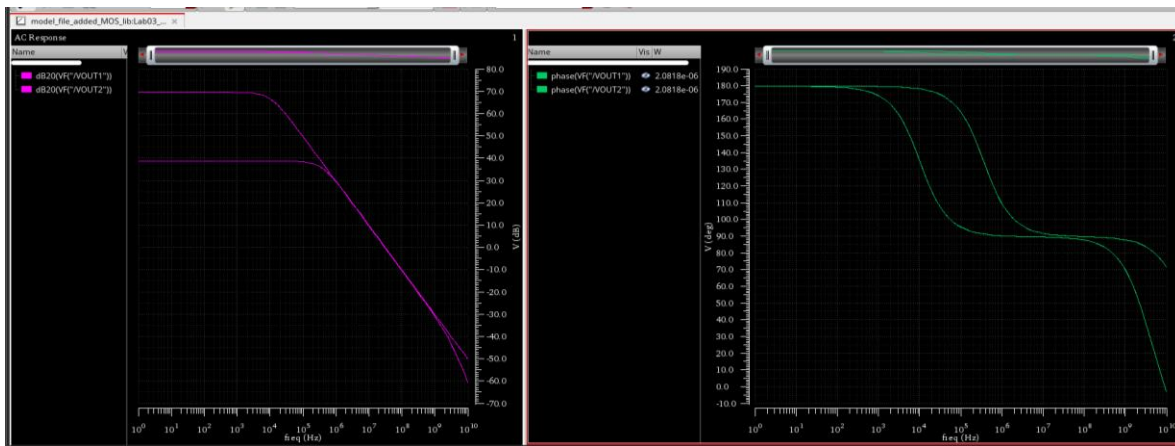

## AC analysis.

for The Common Source :

$$\begin{aligned}
 \text{gain} &= |A_v| = g_m r_o^{\text{intrinsic}} \\
 &= \frac{199.7 \times 10^{-6}}{2.253 \times 10^{-6}} \\
 &= 88.637 \text{ V/V} \\
 &= 38.952 \text{ dB}
 \end{aligned}$$

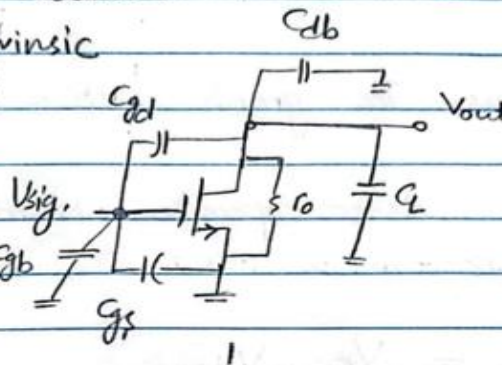

$$\omega_{\text{Pout}} \sim \text{BW} = \frac{1}{r_o (C_L + C_{db} + C_{gs} (1 + \frac{1}{A_v}))}$$

$$= 2.246 \text{ Mrad/sec} \times 10^6 \text{ rad/sec}$$

$$f_{\text{BW}} = \frac{\omega_{\text{Pout}}}{2\pi} = 357.77 \text{ KHz}$$

$$\text{GBW} = \text{gain} \times \omega_{\text{Pout}} = 31.783 \times 10^6$$

$$\text{UGF} \sim \text{GBW} = 31.783 \times 10^6 \text{ MHz}$$

A Method to get  $f_u$  is that  $|A_v| = 1$

$$A_v = G_m R_{\text{out}} \therefore R_{\text{out}} = \frac{1}{G_m}$$

$$\therefore \omega_{\text{Pout}} = \frac{g_m}{C_L + C_{db} + C_{gs} (1 + \frac{1}{A_v})}$$

Don't forget the body effect

For The Cascode

$$R_{out} = r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2}$$

$$\bar{G}_m = \frac{i_{sc}}{V_{sig}} \approx -g_{m1}$$

$$R_{out} = 16.002 \text{ M}\Omega$$

$$\therefore \text{Gain} = -g_{m1} (r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2})$$

$$= -3086.7 \text{ V/V}$$

$$\text{dB} \Rightarrow 69.789 \text{ dB}$$

$\therefore V_x$  is a Low input node  
it will not be dominant

$$\therefore BW \approx \omega_{pout} =$$


$$R_{out} [C_L + C_{db2} + C_{gd2}]$$

$$= 62320.396 \text{ rad/s}$$

$$f_{BW} = 9.923 \text{ kHz}$$

$$GBW = 30.629 \text{ M}$$

$$f_u \approx GBW = 30.629 \text{ MHz}$$

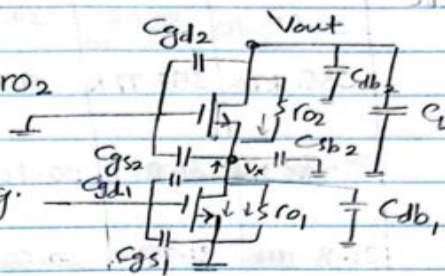

$$i_{sc} + \frac{V_x}{r_{o1}} + g_{m1} V_{sig} = 0$$

$$V_x = -i_{sc} r_{o1} - g_{m1} r_{o1} V_{sig}$$

$$\therefore -g_{m2} V_x - \frac{V_x}{r_{o2}} + i_{sc} = 0$$

$$i_{sc} = (g_{m2} + \frac{1}{r_{o2}}) (-i_{sc} r_{o1} - g_{m1} r_{o1} V_{sig})$$

$$i_{sc} (1 + g_{m2} r_{o1} + \frac{r_{o1}}{r_{o2}}) =$$

$$\text{neglected body effect} \quad -g_{m1} r_{o1} (g_{m2} + \frac{1}{r_{o2}}) V_{sig}$$

$$\therefore G_m = \frac{-g_{m1} r_{o1} (g_{m2} + \frac{1}{r_{o2}})}{1 + g_{m2} r_{o1} + \frac{r_{o1}}{r_{o2}}}$$

$$= -1.9289 \times 10^{-4}$$

CS Cascode

	simu.	hand.	simu.	hand.
DC gain	38.95 dB	38.95 dB	69.79 dB	69.789 dB
BW	385 kHz	357.77 K	9.901 K	9.923 K
UGF	31.705 MHz	31.783 M	30.705 M	30.62 M
GBW	31.8 MHz	31.783 M	30.62 M	30.62 M

\* we used (octC + Millers) approx. for hand analysis



My comment on the previous data:

→ The addition of The Cascode increased The output resistance to a high value Thus it increased the gain but at the same lowered The dominant pole Thus lowered The Bandwidth.

with Cascode gain  $\uparrow$  BW  $\downarrow$  swing  $\downarrow$

to get  $f_u$  :  $|A_v| = G_m R_{out} = 1$

$$\therefore R_{out \text{ unity}} = \frac{1}{G_m}$$

$$\therefore f_u = \frac{1}{2\pi} \times \frac{G_m}{C_L + C_{db2} + C_{gd2}}$$

In Common Source

$$\text{Gain} \times \text{BW} \approx G_{m1} R_{out} \times \frac{1}{R_{out} C_{out}} \approx \frac{G_{m1}}{C_{out}}$$

In Cascode

$$\text{GBW} = G_m R_{out} \times \frac{1}{R_{out} C_{out}} \approx \frac{G_m}{C_{out}}$$

Cascode doesn't change The GBW much because The output pole is dominant for both topologies and thus if The gain inc. by a factor  $K$  with The Cascode the gain will decrease by the same factor thus GBW would be constant

GBW is independent of The output impedance

~~Cascode~~ Cascoding might change the GBW if the dominant pole changed from the output to the input but this diff didn't happen here.


## PART 3 [Optional]: Cascode for BW

### 1. OP Analysis

- ✓1) Create a new cell and schematic. Copy the old schematic instances to the new one. Make the following modifications: remove the feedback resistance, set  $C_L = 1fF$ , replace the current source with a resistor  $R_D$ , make the signal source resistance =  $10M\Omega$  (remove the AC value). Set  $V_{GS}$  of the input device as calculated in Part 1.
- 2) Calculate  $R_D$  analytically such that the voltage drop on it is  $\approx V_{DD}/2$  (the current remains roughly the same as in Part 2 because we are using the same  $V_{GS}$ ).
- 3) Note that the DC voltage of the output node is set by the resistance ( $R_D$ ); thus, we don't need a feedback loop as in the previous case.
- 4) Simulate the DC OP point of the new CS and cascode amplifiers. Add monitors and report a snapshot showing the following parameters for M1, M2 and M3 in addition to DC node voltages clearly annotated.

ID
VGS
VDS
VTH
VDSAT
GM
GDS
GMB
CDB
CGD
CGS
CSB
Region

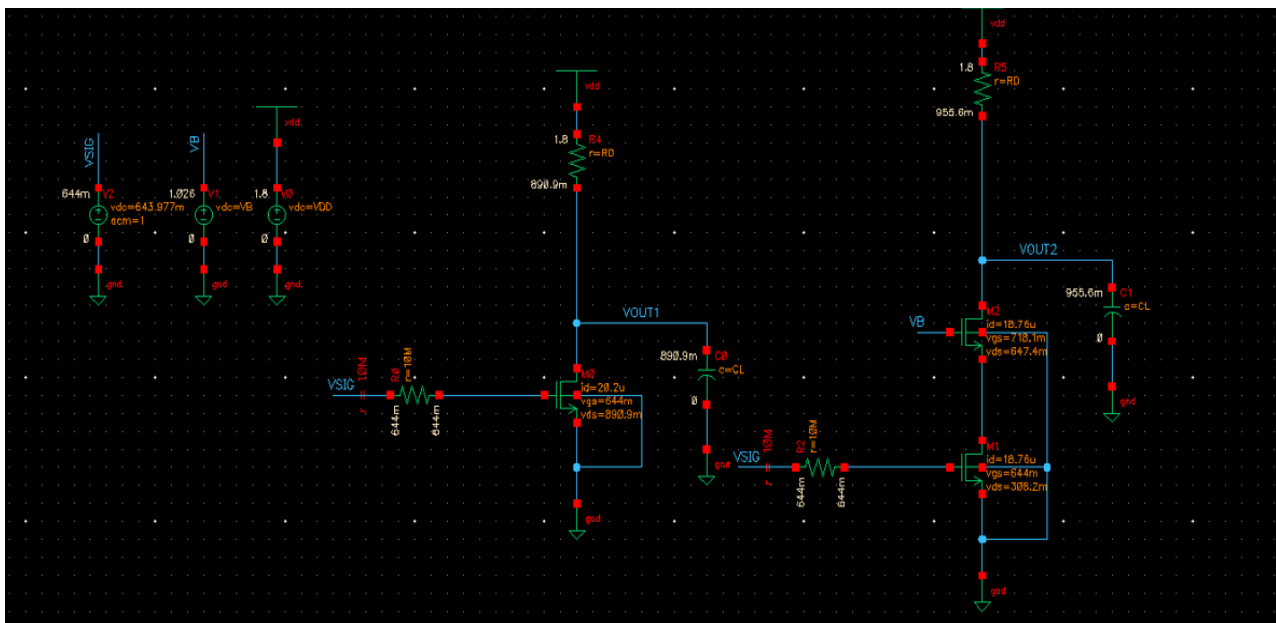- 5✓ Check that all transistors operate in saturation.





1	
W	2.082E-6
M0:ld	20.20E-6
M0:vgS (V)	644.0E-3
M0:vds (V)	890.9E-3
M0:vth (V)	440.3E-3
M0:vdSat (V)	155.3E-3
M0:gm	201.3E-6
M0:gds	2.083E-6
M0:gmb	54.34E-6
M0:cdb	-1.672E-15
M0:cgd	-981.6E-18
M0:cgs	-7.494E-15
M0:csb	-3.744E-15
M0:region	2

1	
W	2.082E-6
M1:ld	18.76E-6
M1:vgS (V)	644.0E-3
M1:vds (V)	308.2E-3
M1:vth (V)	444.6E-3
M1:vdSat (V)	152.4E-3
M1:gm	190.6E-6
M1:gds	3.942E-6
M1:gmb	51.61E-6
M1:cdb	-1.903E-15
M1:cgd	-1.007E-15
M1:cgs	-7.502E-15
M1:csb	-3.735E-15
M1:region	2

1	
W	2.082E-6
M2:ld	18.76E-6
M2:vgS (V)	718.1E-3
M2:vds (V)	647.4E-3
M2:vth (V)	530.5E-3
M2:vdSat (V)	154.8E-3
M2:gm	195.9E-6
M2:gds	2.220E-6
M2:gmb	47.45E-6
M2:cdb	-1.657E-15
M2:cgd	-982.0E-18
M2:cgs	-7.427E-15
M2:csb	-3.321E-15
M2:region	2



$$R_D = \frac{V_{DS}}{I_B} \quad \therefore \quad R_D = \frac{0.9}{20 \mu A} = 45 \text{ k}\Omega$$

5) All transistors operate in subthreshold since they are all region 2

## 2. AC Analysis

- 1) Perform AC analysis (1Hz:10GHz, logarithmic, 10points/decade) to simulate gain and bandwidth.
- 2) Use calculator to create expressions for circuit parameters (DC gain, BW, GBW, and UGF) and export them to adexl.
- 3) Report the Bode plot (magnitude) of CS and cascode **appended on the same plot.**
- 4) Using small signal parameters from OP simulation, perform hand analysis to calculate DC gain, BW, and GBW of both circuits.
- 5) Report a table comparing the DC gain, BW, UGF, and GBW of both circuits from simulation and hand analysis. Comment on the results.

Test	Output	Nominal	Spec	Weight	Pass/Fail
model_file_added_MOS_IbLab03_Part_Optional1	dB20(V("VOUT1"))				
model_file_added_MOS_IbLab03_Part_Optional1	ymax(dB20(V("VOUT1")))	18.36			
model_file_added_MOS_IbLab03_Part_Optional1	mag(V("VOUT1"))				
model_file_added_MOS_IbLab03_Part_Optional1	ymax(mag(V("VOUT1")))	8.281			
model_file_added_MOS_IbLab03_Part_Optional1	bandwidth(V("VOUT1")) 3 %	933.5k			
model_file_added_MOS_IbLab03_Part_Optional1	gainBwProd(V("VOUT1"))	7.748M			
model_file_added_MOS_IbLab03_Part_Optional1	dB20(V("VOUT2"))				
model_file_added_MOS_IbLab03_Part_Optional1	ymax(dB20(V("VOUT2")))	18.52			
model_file_added_MOS_IbLab03_Part_Optional1	mag(V("VOUT2"))				
model_file_added_MOS_IbLab03_Part_Optional1	ymax(mag(V("VOUT2")))	8.429			
model_file_added_MOS_IbLab03_Part_Optional1	bandwidth(V("VOUT2")) 3 %	1.625M			
model_file_added_MOS_IbLab03_Part_Optional1	gainBwProd(V("VOUT2"))	13.73M			

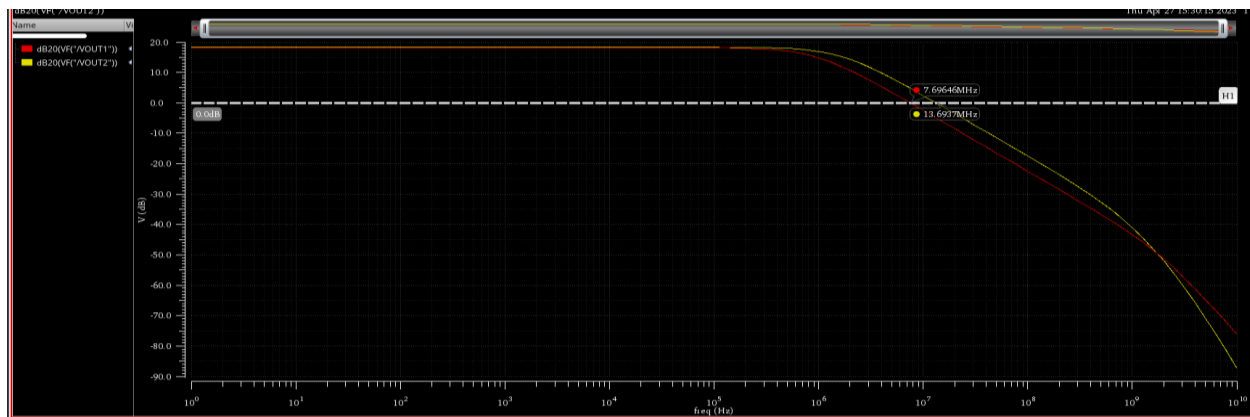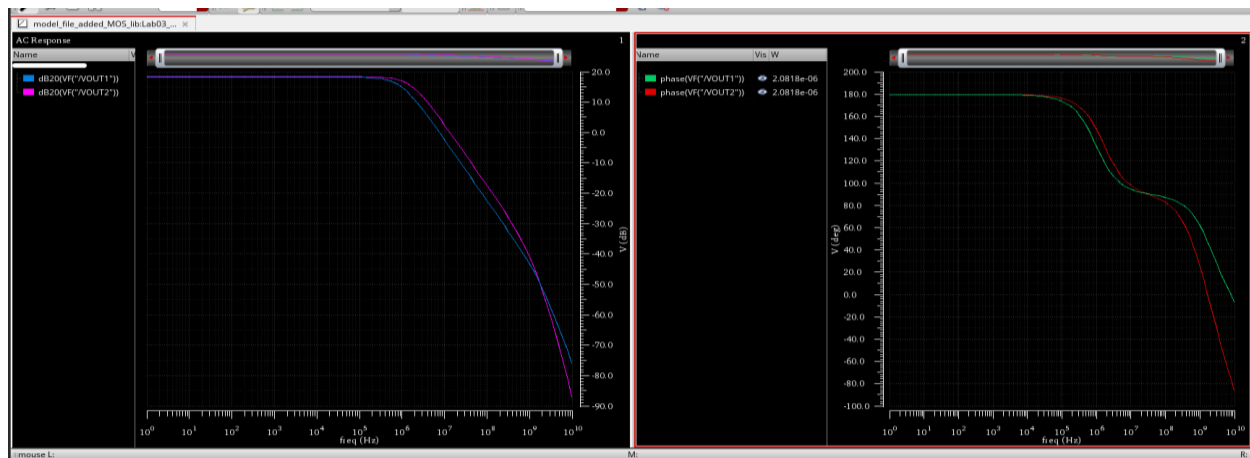

for The Common Source : As calculated in the  
Previous part

$$\text{Gain} = -g_m(r_o \parallel R_D)$$

$$r_o = \frac{1}{2.083 \times 10^{-6}} = 480.076 \text{ K}\Omega$$

$$= 201.3 \times 10^{-6} \times 41.143 \times 10^3 = -8.282 \text{ V/V}$$


$$= 18.3628 \text{ dB}$$

$$\omega_{p_{out}} = \frac{1}{R_{out} (C_L + C_{db} + C_{gd} (1 + \frac{1}{A_v}))}$$

$$= \frac{1}{41143.42 (10^{-15} + 1.67 \times 10^{-15} + 981.6 \times 10^{-18} (1 + \frac{1}{8.28}))}$$

$$= 6.4467 \times 10^9 \text{ rad/sec}$$

$$= 1.0265 \text{ GHz}$$

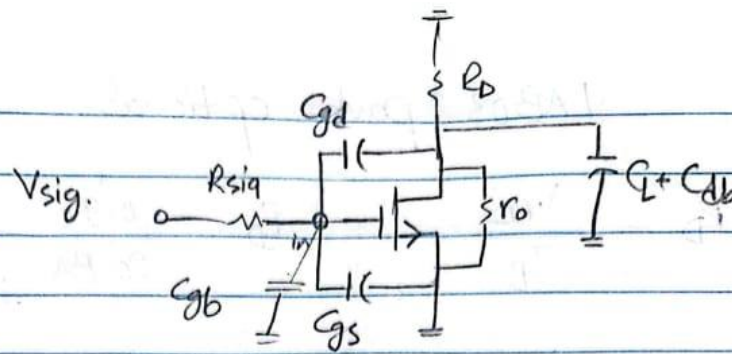

$$\omega_{p_{in}} = \frac{1}{R_{sig} (C_{gs} + C_{gb} + C_{gd} (1+A))}$$

$$= \frac{1}{10 \times 10^6 \left[ \frac{7.494}{10^{15}} + \frac{981.6}{10^{18}} (1 + 8.282) \right]}$$

$$= 6.0222 \times 10^6 \text{ rad/sec}$$

$$BW \approx 958.9 \text{ kHz}$$

input pole will be the dominant pole

$$BW = \frac{1}{\frac{1}{\omega_{p_{in}}} + \frac{1}{\omega_{p_{out}}}} \approx \omega_{p_{in}}$$

$$GBW = 7.9416 \text{ MHz}$$

$$f_u \approx GBW = 7.941 \text{ MHz}$$



Cascode Circuit:

$$R_{out} = R_D \parallel (r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2}) R_D$$


$$= 44.929 \text{ k}\Omega$$

$$G_m \approx -g_{m1}$$

$$\text{Gain} = G_m R_{out}$$

$$= -8.563 \text{ V/V}$$

$$= 18.6529 \text{ dB}$$

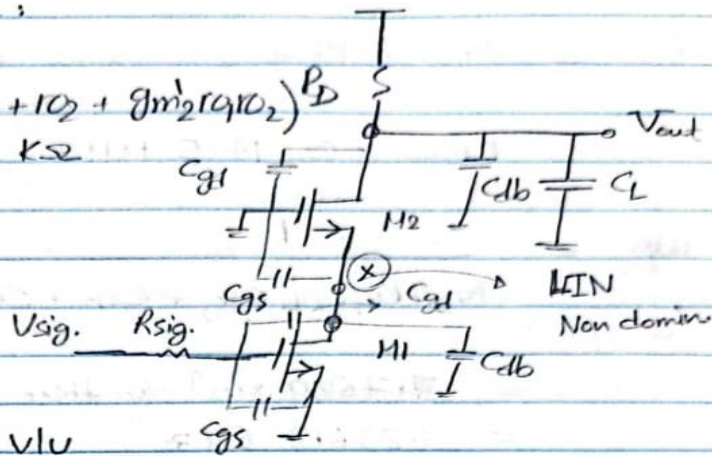

The BW will be determined by  $\omega_{p_{in}}$ ,  $\omega_{p_{out}}$

$$\omega_{p_{out}} = \frac{1}{R_{out} (C_{db2} + C_{L2} + C_{gd2})} = 6.11633 \times 10^9 \text{ rad/sec}$$

$$= 973.93 \text{ MHz}$$

$$\omega_{p_{in}} = \frac{1}{R_{sig} (C_{gs} + C_{g1} (1 + A_o))}$$

$$A_o = -g_{m1} (r_{o1} \parallel R_{Lfs})$$

$$R_{Lfs} = \frac{1}{g_{m2}} \left( 1 + \frac{R_D}{r_{o2}} \right)$$

$$= 1.7 \text{ MHz}$$

$$R_{Lfs} = 4519.827 \Omega$$

$$A_o = 0.84639 \text{ V/V}$$

$$BW = \frac{1}{\frac{1}{\omega_{p_{in}}} + \frac{1}{\omega_{p_{out}}} + \frac{1}{\omega_{p_x}}} \approx 1.697 \text{ MHz}$$

$$GBW = 14.531 \text{ MHz}$$

$$f_u \approx GBW \approx 14.5 \text{ MHz}$$

$$\omega_{p_x} = \frac{1}{(r_{o1} \parallel R_{Lfs}) [C_{gs2} + C_{db1} + C_{sb2} + C_{gs1} (1 + \frac{1}{A_o})]}$$

$$4439.9$$

$$= 7.7629 \times 10^9 \text{ rad/sec}$$

$$= 1.23613 \text{ GHz}$$

Table and comment:

		Cascode			
		Simul.	Hand	Simul.	Hand
CS	DC gain	18.36 dB	18.362 dB	18.52 dB	18.6529 dB
	BW	933.5 K	958.9 K	1.625 M	1.697 MHz
	UGF	7.696 M	7.941 M	13.693 M	14.5 MHz
	GBW	7.748 M	7.941 M	13.73 M	14.5 MHz

→ we used the OCTC + Millers technique

Comment

adding The cascode didnot change the gain much because  $R_D$  was too small that it prevents the cascode from increasing the

output impedance since it's parallel to it thus the gain didnot change.

as for the Bandwidth, the dominant pole is the input pole and adding the cascode decreases the Miller's effect on the input pole thus caused bandwidth extension.

This caused the gain bandwidth product to change.

THE END